

2012-1: Transmission Lines and Antennas





Javier Leonardo Araque Quijano

Of: 453 – 204

Ext. 14083

jlaraqueq@unal.edu.co

Transmission Lines

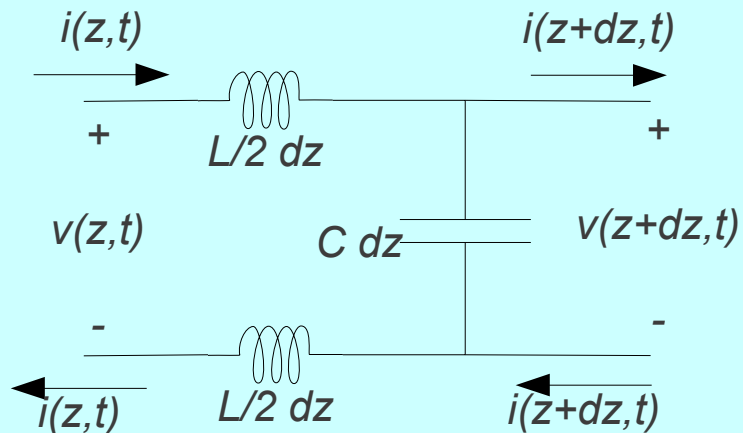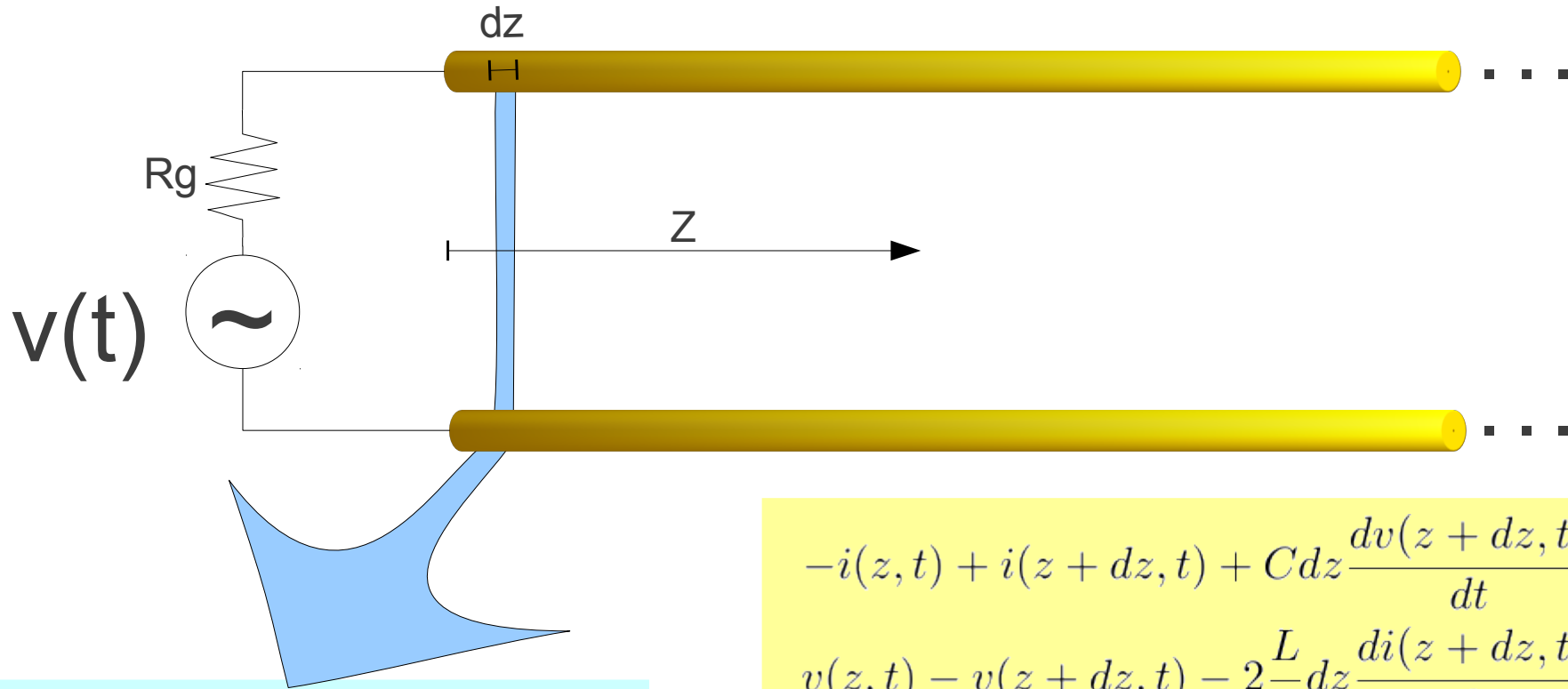

$$-i(z,t) + i(z+dz,t) + Cdz \frac{dv(z+dz,t)}{dt} = 0$$

$$v(z,t) - v(z+dz,t) - 2\frac{L}{2}dz \frac{di(z+dz,t)}{dt} = 0$$

$$dz \rightarrow 0$$

Telegrapher's equations

$$\left[\begin{aligned} \frac{\partial i(z,t)}{\partial z} + C \frac{\partial v(z,t)}{\partial t} &= 0 \\ \frac{\partial v(z,t)}{\partial z} + L \frac{\partial i(z,t)}{\partial t} &= 0 \end{aligned} \right]$$

Waves in Transmission Lines

- Partial derivation of equations above (one wrt t, other wrt z followed by substitution of the element with crossed differentials) results in identical (wave) equations for $v(z,t)$ and $i(z,t)$:


$$\begin{aligned}\frac{\partial^2 v(z,t)}{\partial z^2} - LC \frac{\partial^2 v(z,t)}{\partial t^2} &= 0 \\ \frac{\partial^2 i(z,t)}{\partial z^2} - LC \frac{\partial^2 i(z,t)}{\partial t^2} &= 0\end{aligned}$$

Units $(s/m)^2$,
the inverse of a
square velocity

- General solutions have the form:

$$\begin{aligned}v(z,t) &= V^+ f^+ \left(t - \frac{z}{v} \right) + V^- f^- \left(t + \frac{z}{v} \right) \\ i(z,t) &= \frac{V^+}{Z_c} f^+ \left(t - \frac{z}{v} \right) - \frac{V^-}{Z_c} f^- \left(t + \frac{z}{v} \right) \\ Z_c &= \sqrt{\frac{L}{C}} \quad v = \frac{1}{\sqrt{LC}}\end{aligned}$$

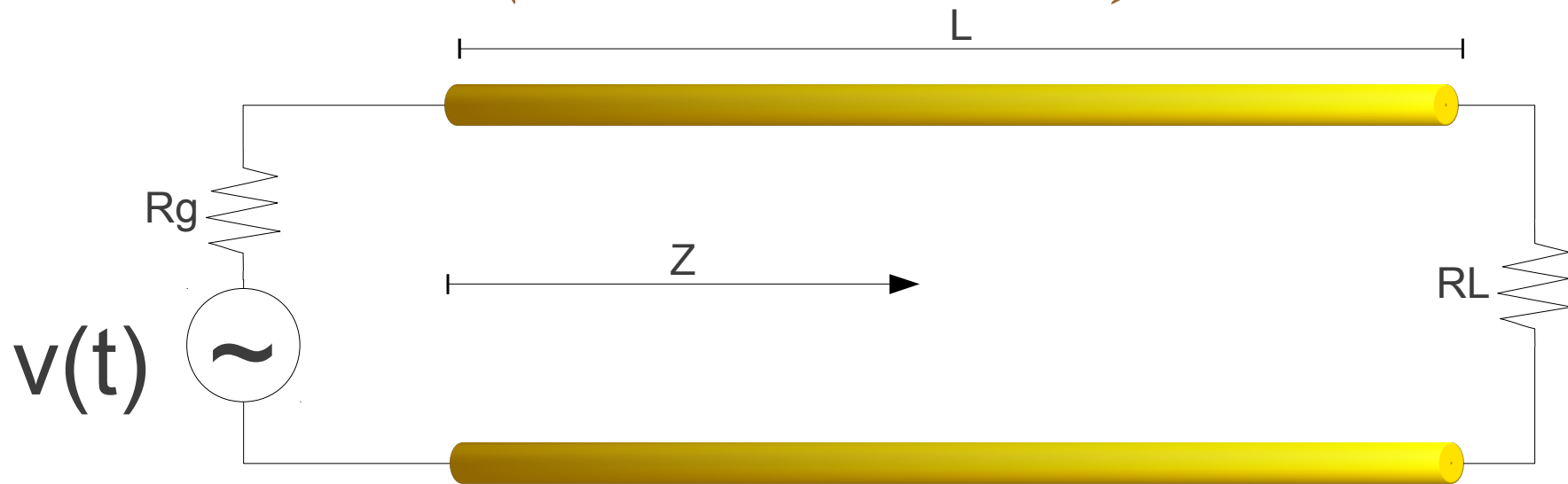
Terminated Transmission Lines (Time Domain)



In general both forward and backward waves are required to satisfy boundary conditions (voltage/current ratio at lumped loads). Whenever Z_c and the terminating load are different, a reflected wave is generated, the reflection coefficient is:

$$\Gamma_L = \frac{R_L - Z_c}{R_L + Z_c} \quad \Gamma_g = \frac{R_g - Z_c}{R_g + Z_c}$$

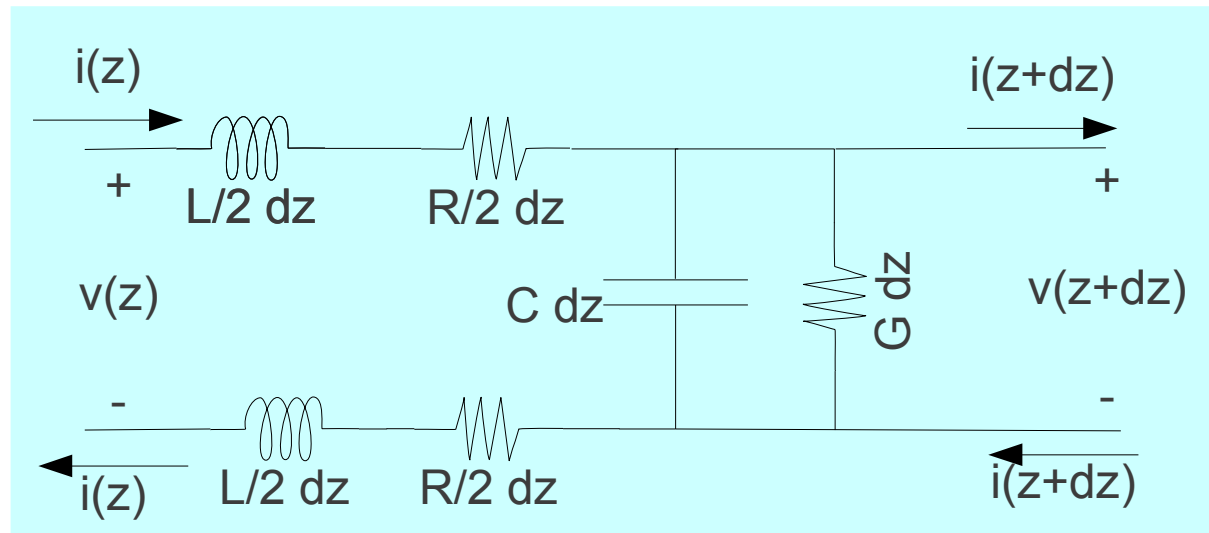Lossy Transmission Lines (Frequency Domain)



$$v(z) = V^+ e^{-\gamma z} + V^- e^{\gamma z}$$


$$i(z) = \frac{V^+}{Z_c} e^{-\gamma z} - \frac{V^-}{Z_c} e^{\gamma z}$$

$$\gamma = \sqrt{(R + j\omega L)(G + j\omega C)}$$

$$Z_c = \sqrt{\frac{R + j\omega L}{G + j\omega C}}$$

Generic lossy lines are:
Dispersive = phase velocity
depends on frequency
Distorting = Attenuation
constant depends on frequency

Terminated Lossy Line (Frequency Domain)

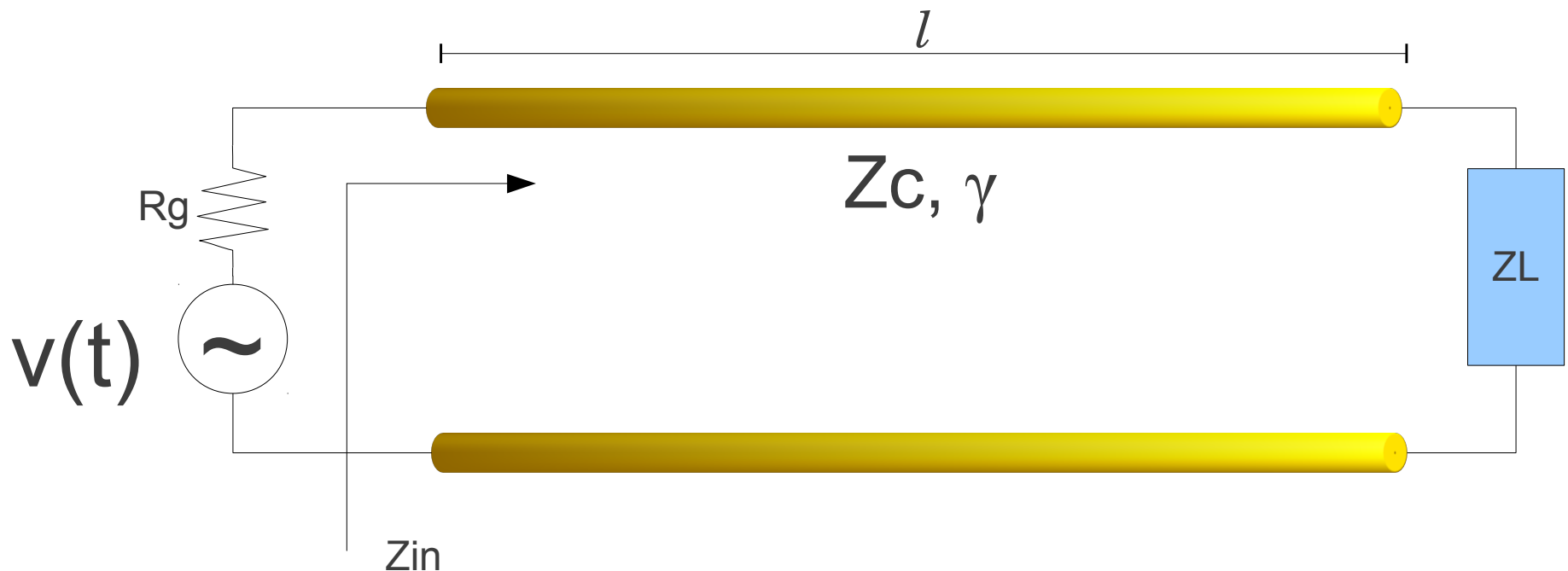

$$Z_{in} = Z_C \frac{Z_L + Z_C \tanh(\gamma l)}{Z_C + Z_L \tanh(\gamma l)}$$

Important parameters

- Wavelength
- Phase velocity
- Power flow
- Terminated lines, load matching
- Reflection coefficient
- Standing Wave Ratio (SWR)
- Attenuation constant (perturbation technique)