


2012-1: Transmission Lines and Antennas



Javier Leonardo Araque Quijano
 Of: 453 – 204
 Ext. 14083
 jlaraqueq@unal.edu.co

Scattering Matrix

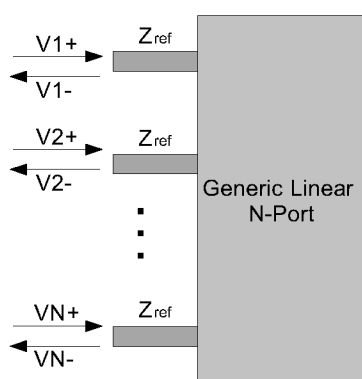The Scattering Matrix (S-Matrix) is the preferred representation at microwave frequencies as voltage/currents are not well defined in all cases as required for usual matrix representations (Z, Y, etc.)



$$\begin{bmatrix} v_1^- \\ \vdots \\ v_N^- \end{bmatrix} = \begin{bmatrix} S_{1,1} & \cdots & S_{1,N} \\ \vdots & & \vdots \\ S_{N,1} & \cdots & S_{N,N} \end{bmatrix} \begin{bmatrix} v_1^+ \\ \vdots \\ v_N^+ \end{bmatrix}$$

$$\mathbf{v}^- = \mathbf{S} \mathbf{v}^+$$

The $S_{m,n}$ element is obtained as follows:

$$S_{m,n} = v_m^- / v_n^+ \text{ when } v_p^+ = 0 \quad \forall p \neq n$$

i.e. Feed only nth port, terminate all other ports in a matched load.

Properties of the S-Matrix

$\mathbf{S} = \mathbf{S}^T$ for reciprocal networks

$\sum_{k=1}^N |S_{k,n}|^2 \leq 1 \quad \forall n$ for passive networks
i.e. norm of column vectors is always ≤ 1
(equality holds for lossless networks)


$$\mathbf{S} = (\mathbf{Z}/Z_0 + \mathbf{I})^{-1} (\mathbf{Z}/Z_0 - \mathbf{I}) \quad \mathbf{Z} = Z_0 (\mathbf{I} + \mathbf{S}) (\mathbf{I} - \mathbf{S})^{-1}$$

$$\mathbf{S} = (\mathbf{I} + \mathbf{Y}/Y_0)^{-1} (\mathbf{I} - \mathbf{Y}/Y_0) \quad \mathbf{Y} = Y_0 (\mathbf{I} - \mathbf{S}) (\mathbf{I} + \mathbf{S})^{-1}$$

where \mathbf{Z} and \mathbf{Y} are the impedance and admittance matrices,
 \mathbf{I} is the identity matrix and Z_0 and Y_0 are the port reference
impedance/admittance.

The ABCD matrix

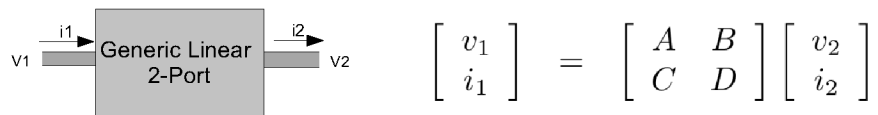- 2-ports are probably the most common device.
- These are usually cascaded.
- ABCD matrix of a cascade of 2-ports is the matrix product of the individual ABCD matrices.



A is the ratio between an applied voltage v_1 and the resulting open-circuit voltage v_2 (i.e. $i_2 = 0$)

B is the ratio between an applied voltage v_1 and the resulting short-circuit current i_2 (i.e. $v_2 = 0$)

C is the ratio between an applied current i_1 and the resulting open-circuit voltage v_2 (i.e. $i_2 = 0$)

D is the ratio between an applied current i_1 and the resulting short-circuit current i_2 (i.e. $v_2 = 0$)

Properties of the ABCD matrix

$$\begin{bmatrix} S_{1,1} & S_{1,2} \\ S_{2,1} & S_{2,2} \end{bmatrix} = \frac{\begin{bmatrix} A + B/Z_0 - CZ_0 - D & 2(AD - BC) \\ 2 & -A + B/Z_0 - CZ_0 + D \end{bmatrix}}{A + B/Z_0 + CZ_0 + D}$$

$$\begin{bmatrix} A & B \\ C & D \end{bmatrix} = \frac{\begin{bmatrix} (1 + S_{1,1})(1 - S_{2,2}) + S_{1,2}S_{2,1} & Z_0\{(1 + S_{1,1})(1 + S_{2,2}) - S_{1,2}S_{2,1}\} \\ \{(1 - S_{1,1})(1 - S_{2,2}) - S_{1,2}S_{2,1}\}/Z_0 & (1 - S_{1,1})(1 + S_{2,2}) + S_{1,2}S_{2,1} \end{bmatrix}}{2S_{2,1}}$$

- For reciprocal networks, determinant of ABCD matrix $AD - BC = 1$
- For symmetrical networks $A = D = \pm \sqrt{1 + BC}$